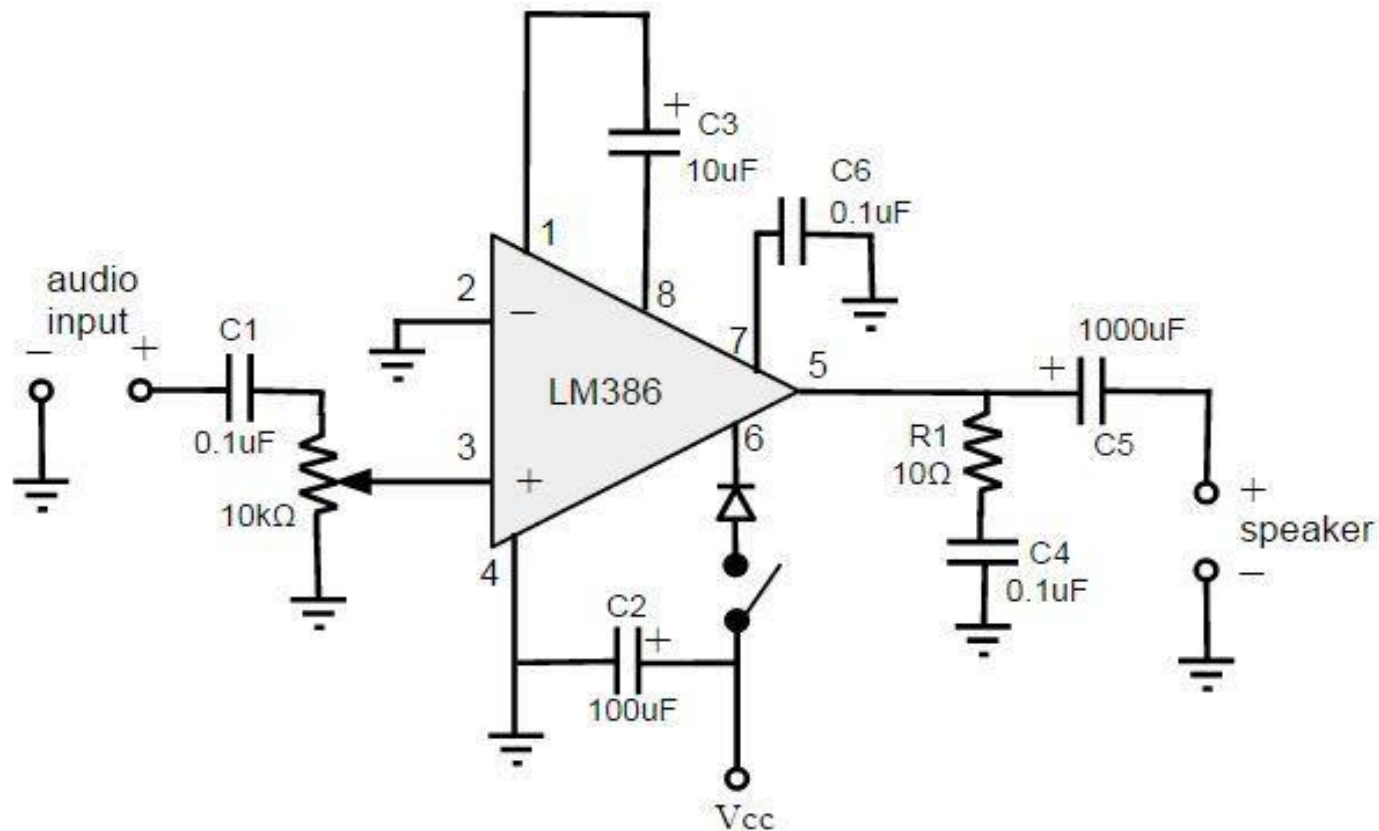


Lab 2: Analog Circuits

Korey Huynh
Harrison Trinh
ECE 5 - UC San Diego


Extra Credit: Speaker PCB Circuit

Schematic of Speaker Amplifier




Schematic File

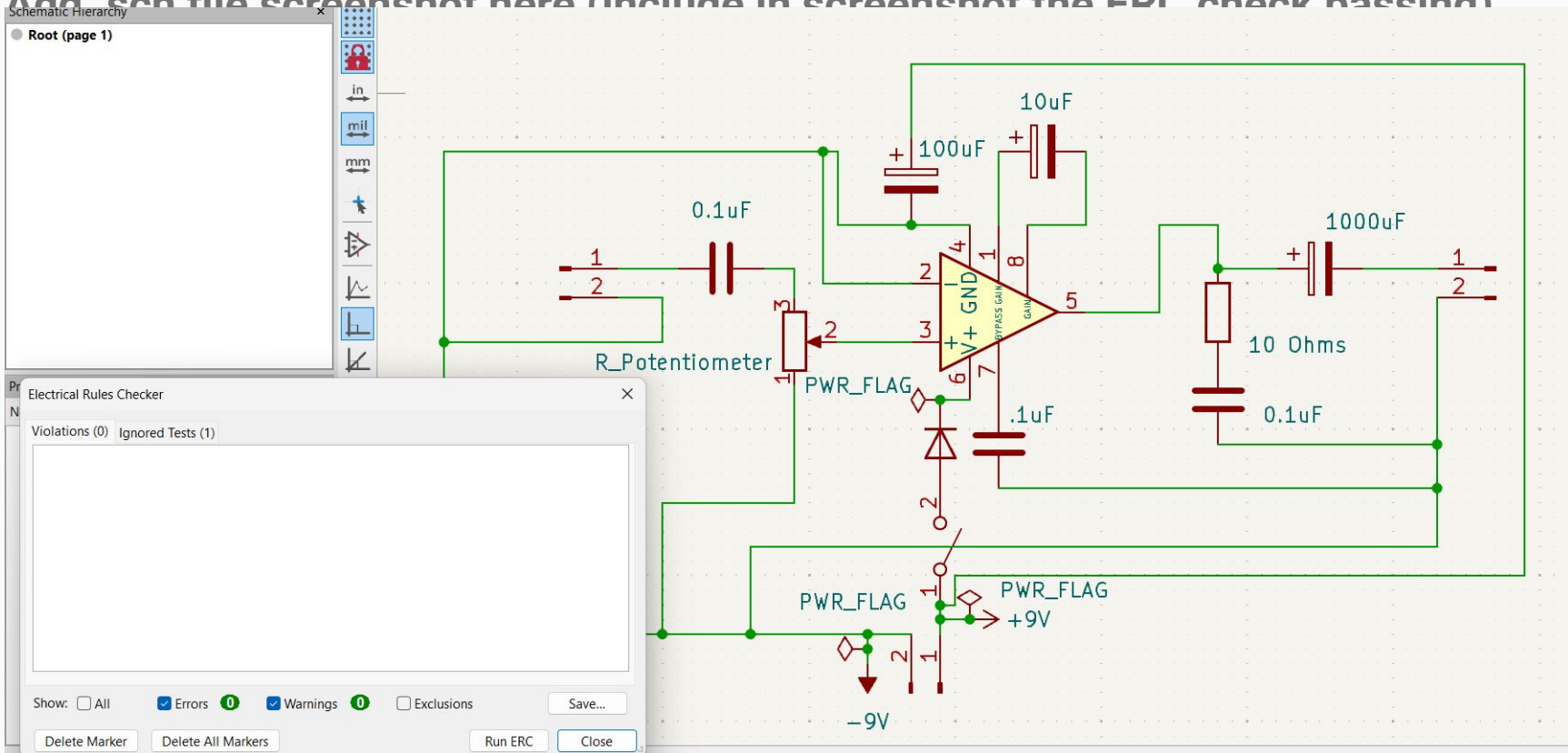Add screenshot here (include in screenshot the EDC check passing)




Board File

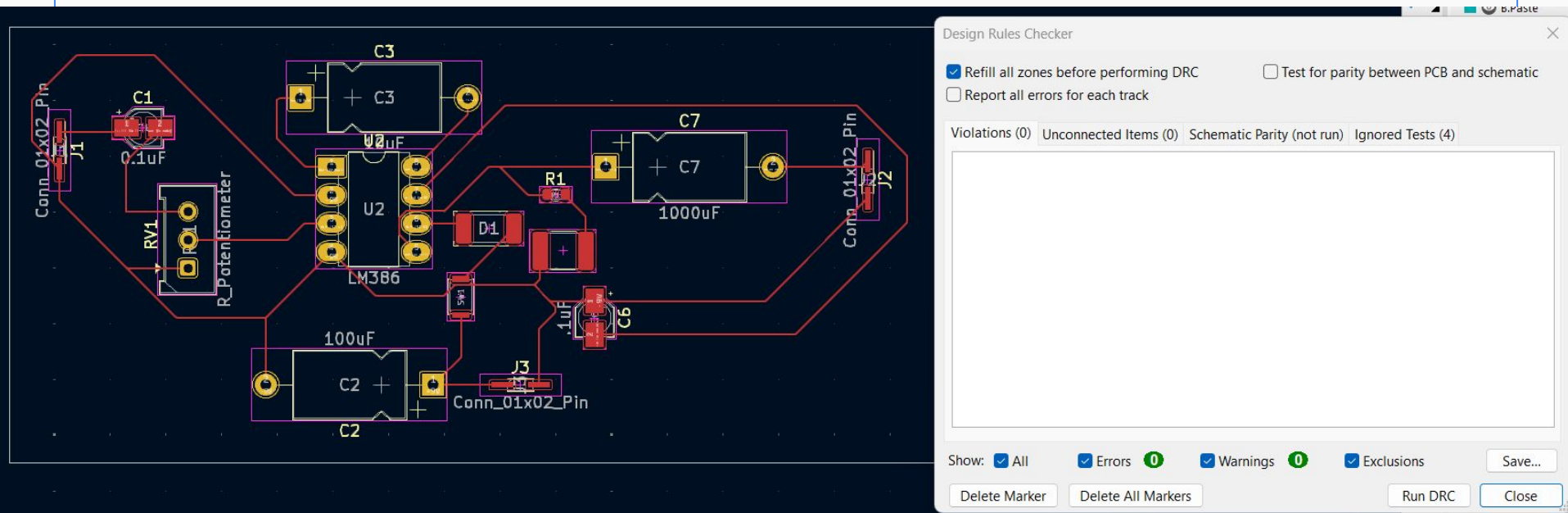Add .pcb file screenshot here (include in screenshot the DRC check passing)



3D PCB Viewer

Add screenshot of 3D PCB Viewer in Kicad

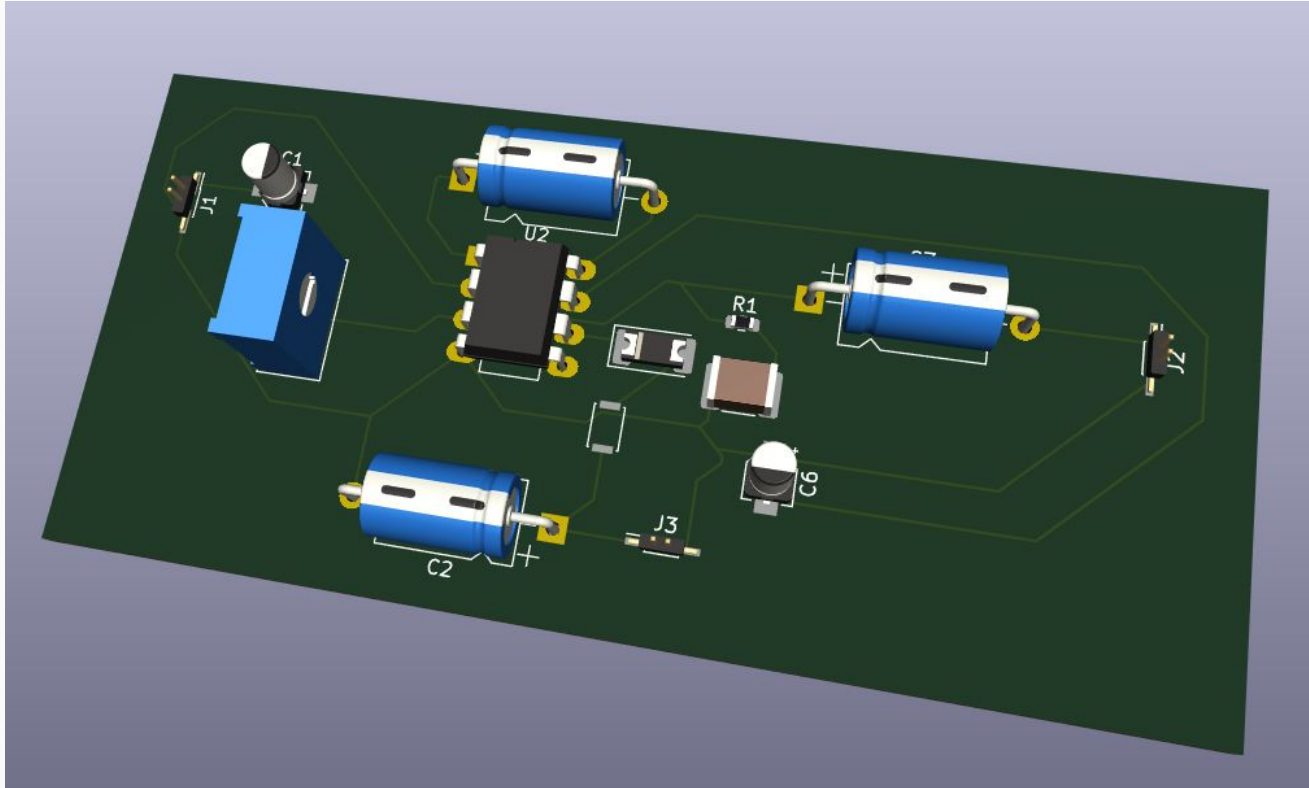

Submission Instructions

- Submit writeup pdf, .sch file, and .pcb file on Gradescope